
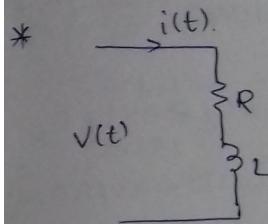



\* winding.

# ELECTRICAL MACHINES.

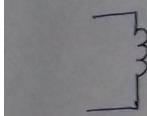


$$V(t) = R i(t) + L \frac{di(t)}{dt}$$

TIME-DOMAIN ANALYSIS.

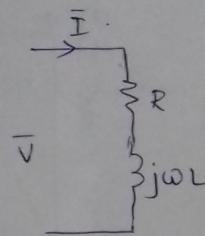

$$\bar{V} = \bar{I}(R + j\omega L)$$

PHASOR-ANALYSIS.

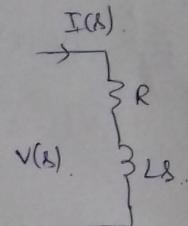

$$V(s) = (R + Ls) I(s)$$

LAPLACE TRANSFORM.

\* Speed of the fan with time.

Time constant =  $\tau = 2s$ .

Time by which the output will be 66% of steady state value.

$$N = N_0 (1 - e^{-t/\tau_0})$$

$N$  = speed,

$N_0$  = final speed.

$$e^{-1} = 36.5\%$$

$$e^{-2} = 13.5\%$$

$$e^{-3} = 5\%$$

$$\tau = \frac{J}{B}$$

$$e^{-4} = 2\%$$

$J$  = Moment of Inertia ( $\text{kgm}^2$ ),

$$e^{-5} = 1\%$$


$B$  = Friction coefficient.

$T \rightarrow \text{N.m.}$

$$T = B \cdot \omega$$

$$\text{N.m.} = B \cdot \frac{\text{rad}}{\text{s}}$$
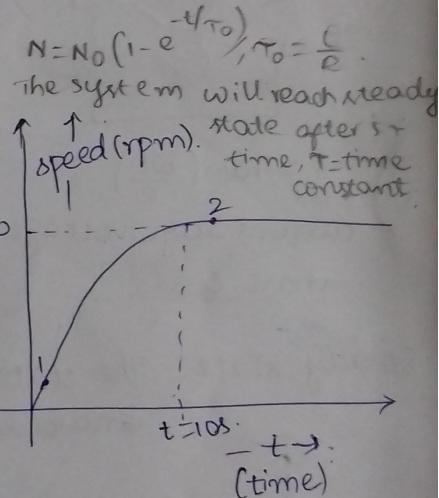
$$\Rightarrow B = \frac{\text{N.m.s}}{\text{rad}}$$



$$I_1 > I_2$$

$$\text{Torque}(r) = \frac{J}{B}$$

$$\text{Torque}(r) = \frac{J}{B}$$




$$V = iR + L \frac{di}{dt}$$

$$V - iR = L \frac{di}{dt}$$


$$\frac{1}{R} (V - iR) di = \frac{1}{L} dt$$

$$\frac{1}{R} \int (V - iR) di = \frac{1}{L} \int dt$$

$$i = V(1 - e^{-R/L t})$$

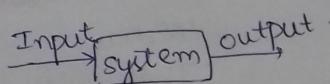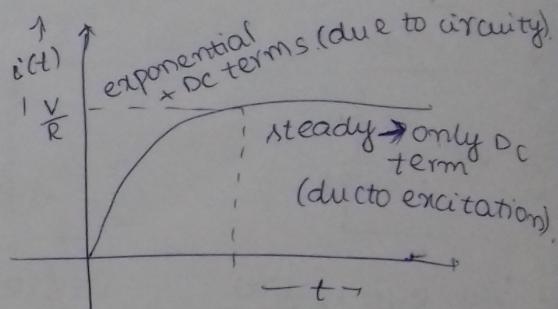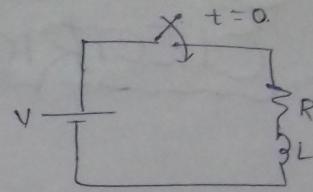


\*

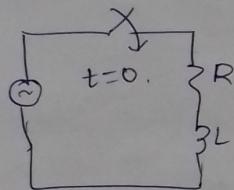


$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

current lags voltage by phase  $\phi$ .

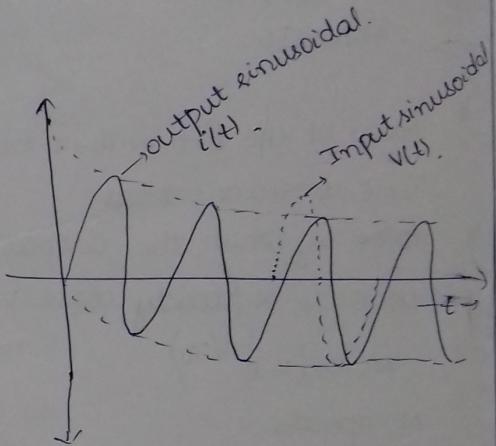

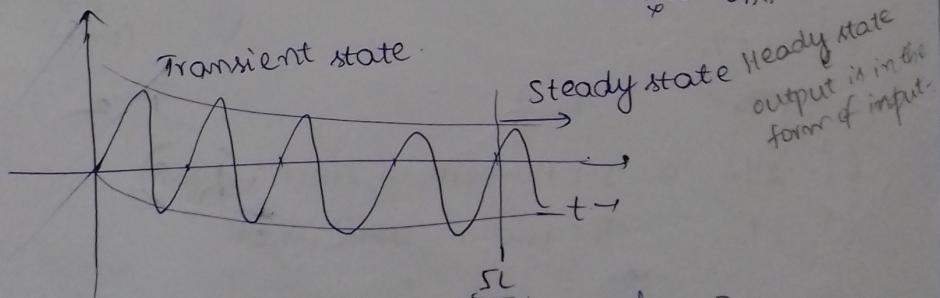Steady state :- The state at which the final response is sinusoidal that of the excitation.



$$\tau = 4R$$

$$f = 50 \text{ Hz}$$

$$\frac{2\pi}{T} = \frac{2\pi}{4R} = \frac{1}{50}$$

$$T = 4R \quad f = \frac{1}{4R} \quad \text{Four time period} \quad (\therefore \text{Four cycles})$$

$$\therefore 5 \times \frac{L}{R} = 4 \times \frac{1}{50} \quad R = 10 \Omega$$

$$\frac{5}{10} \times L = \frac{4}{50} \Rightarrow L = \frac{4}{25} = 160 \text{ mH} = 0.16 \text{ H}$$

Electrical Time constant =  $16\text{ms}$ , [ $\because t = 80/5 = 16\text{ms}$ ]

Mechanical Time constant =  $2\text{s}$ .

Phase Analysis is applied for.

1. Sinusoidal excitation.

2. Steady-state analysis.

It provides mathematical simplification.

$$\frac{di}{dt} \rightarrow j\omega I \quad \int v(t)dt \rightarrow \frac{\bar{v}}{j\omega}$$


$$t \quad i(t) \quad \frac{di}{dt}$$

$$t_1 \quad I_1$$



$$t_2 \quad I_2 \quad \frac{I_2 - I_1}{t_2 - t_1}$$

$$\vdots \quad \vdots \quad \vdots$$
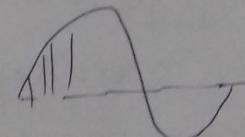
$$t_n \quad I_n \quad \frac{I_n - I_{n-1}}{t_n - t_{n-1}}$$



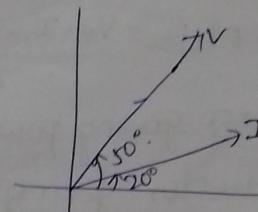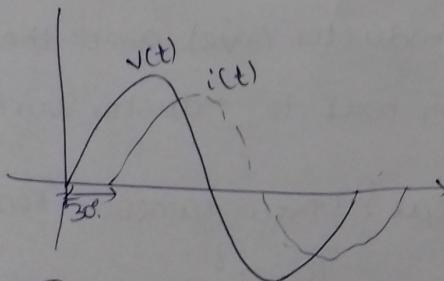\*  $\bar{I} = I \angle \phi_i$ ,  $\bar{V} = V \angle \phi_v$ ,  $f = 50\text{Hz}$ .  
 $= 5 \angle 20^\circ$   $= 10 \angle 50^\circ$ .




Active Power and Reactive Power.

$$P(t) = V(t) \cdot i(t)$$

$V(t) \rightarrow$  Sinusoidal

$$i(t) = \frac{V(t)}{R}$$

Sinusoidal.

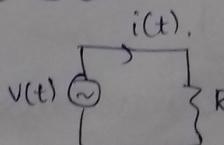


$$\text{Active Power} = V(t) \cdot i(t)$$

Reactive Power?

$$P(t) = V(t) \cdot i(t) = \frac{A^2 \sin^2 \omega t}{R} = \frac{A^2}{2R} (1 - \cos 2\omega t)$$

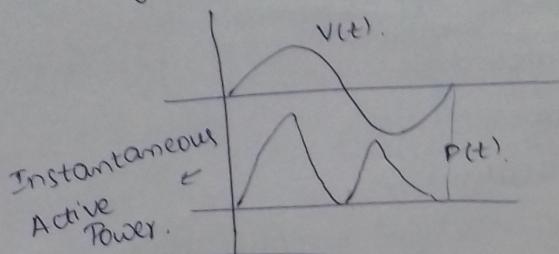When voltage covers 1 cycle, power covers 2 cycles.



$$\boxed{\text{Active Power} = VI \cos \phi}, \quad \text{Active Power} = V I \cos \phi, \quad \text{Reactive Power} = V I \sin \phi.$$

Average power → commonly used:

$$\text{Active Power} = \text{Avg} \{ \text{Instantaneous Active Power} \}.$$

Uni-directional → Active Power.

$$P(t) = V(t) \cdot i(t), \quad \text{Active Power} = \text{Avg} \{ \text{Instantaneous Active Power} \}$$

$$V(t) = V_{\text{ms}} \sin \omega t, \quad \text{Reactive Power} = \text{Peak} \{ \text{Instantaneous Reactive Power} \}$$

$$i(t) = I_{\text{ms}} \sin(\omega t - \pi/2)$$

$$P(t) = \frac{-V_{\text{ms}} I_{\text{ms}} \sin 2\omega t}{2}$$

Source giving power to inductor (+ve), and then inductor giving power back to inductor source (-ve).

$$\text{Reactive Power} = \{ \text{Peak} \{ \text{Instantaneous Reactive Power} \} \}$$

Bi-directional.

$$\boxed{R.P = V I \sin \phi}.$$

\* for RL, state the instantaneous Power, \* instantaneously A.P, instantaneous R.P, A.P, R.P.


\* In steady state, capacitor acts as open circuit  
(after a long time after the switch is closed).

\* Steady state response. → forced response.

\* Steady state response → forced response.  
Transient response → normal response.

$$i(t) = i_m(t) + i_f(t) = \frac{V}{R} e^{-\frac{t}{T}} + \frac{V}{R} - \textcircled{a}$$
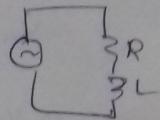
$$= \frac{-V}{R} e^{-\frac{t}{T}} + \frac{V}{R} - \textcircled{b}$$



B)  $V(t) = V_m \sin \omega t$ ,

$$i(t) = \frac{V_m}{|Z|} \sin \phi e^{-\frac{t}{T}} + \frac{V_m}{|Z|} \sin(\omega t - \phi)$$



\* In bulbs, we indicate power by average value.

\* In a bulb, electrical bulb is filled with inert gas.  
temperature of the filament =  $4800^\circ\text{C}$ .

\*  $T_{10}$  of the cigarette, temperature =  $2500^\circ\text{C}$ .

\*  $\Delta R = \alpha \Delta T R_0$

Temperature coefficient:

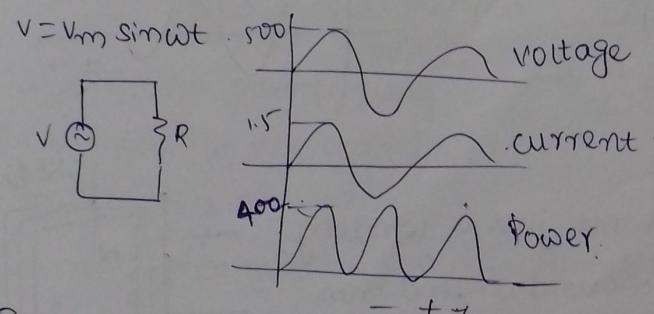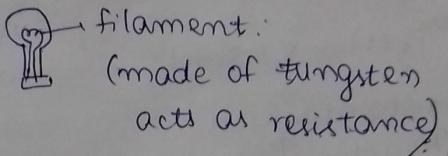

Power → Instantaneous power (unidirectional, +ve).

\* Active Power → Avg { Instantaneous Active Power }  
unidirectional.

Reactive Power → Avg { Instantaneous Reactive Power }  
bidirectional.

\* In R-L circuit,

$$P = V_m I_m \sin \omega t \sin(\omega t - \phi)$$

$$= V_m I_m \left[ \sin^2 \omega t \cos \phi - \sin \omega t \cos \omega t \sin \phi \right]$$

$$= V_m I_m \left[ \frac{(1 - \cos 2\omega t)}{2} \cos \phi - \frac{\sin \phi}{2} \sin 2\omega t \right]$$

$$= V_m I_m \cos \phi \frac{(1 - \cos 2\omega t)}{2} - \frac{\sin V_m I_m \sin 2\omega t \sin \phi}{2}$$

$$V_m = \frac{V}{\sqrt{2}}, I_m = \frac{I}{\sqrt{2}}$$

$$\therefore P = VI \cos \phi (1 - \cos 2\omega t) - VI \sin 2\omega t \sin \phi$$


Instantaneous Power wave form.

$$P_{av} = VI \cos \phi$$

Instantaneous  
In Active Power (Average value)


$$P_r(t) = VI \sin \phi$$

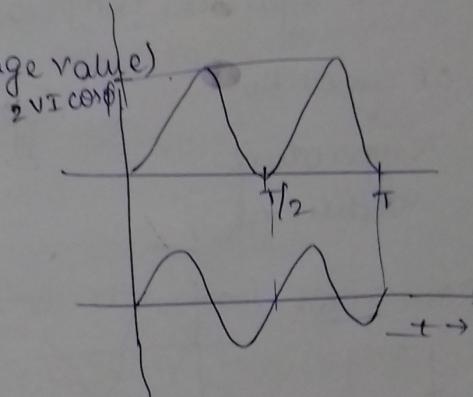Instantaneous  
Reactive Power:  
(Peak Value).



\* Inductor.

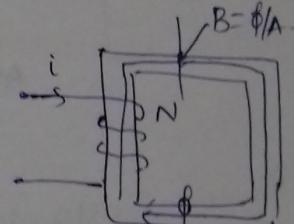Inductor is not just a winding,  
but a coil wound around iron  
core.



Iron core is used because flux will be more.

Magneto Motive Force (MMF) = No. of turns  $\times$  current

$$F = Ni$$

$$MMF. \quad F = \phi \times R$$

Flux  $\downarrow$        $\rightarrow$  reluctance.

$$\text{Magnetic field Intensity } (H) = \frac{\text{MMF}}{\text{length}} = \frac{E}{l} = \frac{N_i}{l}$$

$H \rightarrow \frac{\text{Ampturns}}{\text{meter}}$

$$\text{Electric field Intensity} = \frac{\text{EMF}}{\text{length}}$$

$l = \text{length of the core}$

( $\because$  Along the core, flux has to be distributed).

In case of permanent magnet,

units of  $H \rightarrow \frac{\text{Amp}}{\text{meter}}$  [ $\because$  No. of turns are not considered].

\* Electromagnetic  $\rightarrow$  Permanent magnet.

$\frac{B}{H} = \text{Permeability.}$

$$= \mu$$

$$= \mu_{\text{rel}}$$

where,

$\mu_0 = \text{permeability of free space}$ ,

$$= 4\pi \times 10^{-7}$$

permeability of medium


$\mu_r = \text{relative permeability.}$

For a material,  $\mu_r$  changes.

$$V = iR + L \frac{di}{dt}$$


Inductance goes on changes (Non-linearity = Saturation).

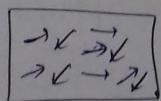\* Initially, in ~~iron core~~ iron cores.



magnetic domain,  
(randomly aligned).

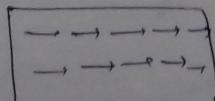After \* Increase the current slowly, after sometime,




Aligned in one direction..

After reaching the above condition, if we further increase the current, there will not be any change in magnetic domain,  $I = \frac{N^2 U A}{l}$ .

\*
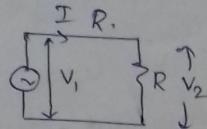
$$\text{Loss} = \frac{(V_1 - V_2)^2}{R}$$



\* AC Voltage.

Magnetic systems store power.

Area under graph is loss of energy.  $\rightarrow$  Hysteresis loss.  
If frequency.

The energy lost is used to do the mechanical work

Residual flux density.

Remanence.

Although you have removed the external field, the magnetic material retains some magnetism.


Coercive force:

Amount of reverse field to be applied so that the magnetic field will lose its magnetism.

Energy lost during 1 cycle of magnetism.  $\rightarrow$  Hysteresis.

$H_c$  = Coercive force,

$B_r$  = Residual flux density.

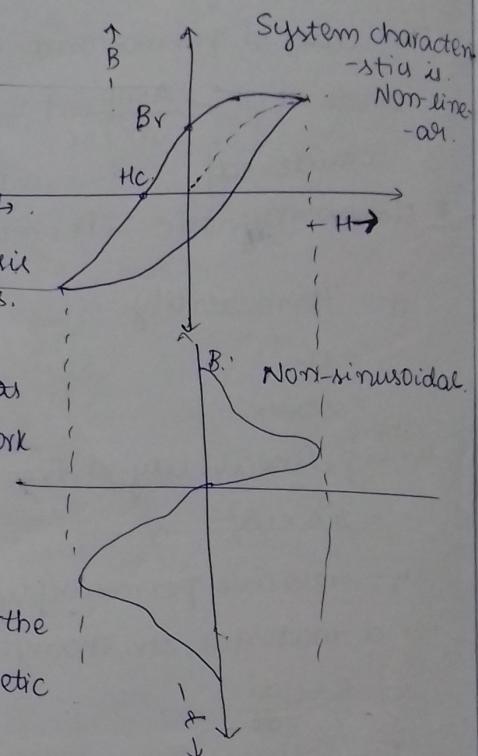

If  
→

Fri  
26-

\*

$B \rightarrow$  input.

If  $B$  and  $H$  are sinusoidal, then, the resulting plot of  $-ph$  has to a straight line passing through origin.  
Input will be voltage (for the transformer).

$$H = \frac{ni}{l}$$

where,  $i$  will be decided by the transformer.

If input is sinusoidal,  $B$  is sinusoidal.

why??

$$V(t) = \frac{N d\phi}{dt}$$

$$= V_m \sin \omega t$$

$$\therefore \phi(t) = \frac{1}{N} \int V(t) dt$$

$\phi(t) \rightarrow$  Sinusoidal,

$B(t) \rightarrow$  Sinusoidal then,

$H(t) \rightarrow$  Non-Sinusoidal.

\* To establish sinusoidal flux in the core, the source has to inject non-sinusoidal input.

Friday.

26-01-18.

Motor :-

Machine which converts electrical to mechanical energy.

\* Machines which provide Mechanical energy are.

Turbine, Engine..

→ Current carrying conductor placed in a magnetic field, it experiences some force..

$$\vec{F} = i \vec{l} \times \vec{B} \rightarrow \text{Lorentz force.}$$

$\vec{l} \rightarrow$  length of the conductor in the direction of current.